

## EE116C/CS151B Homework 2

### Problem 1

As: CPU time = Sum (instruction counts \* CPI) \* seconds/cycles

Thus:

Old CPU time =  $(500m*1+300m*10+100m*3)*CT = 3800m*CT$ ;

New CPU time =  $(500m*0.75*1+300m*10+100m*3)*1.1CT = 4042.5m*CT$ ;

Thus the new CPU time is larger than the old one. So it is not a good design.

### Problem 2

When operating normally, the ALU does subtraction based on the equation:

$$A - B = A + (-B)$$

In those cases, the CarryIn is set to 1 as part of the computation of  $-B$ . Since the malfunction causes CarryIn to be 0, the result for subtraction will always be one less than it should be.

Specifically, instead of computing  $A - B$ , the ALU will compute  $A - B - 1$ .

A user/programmer will observe incorrect results for all instructions that require the ALU to perform subtraction. Specifically:


A) The sub instruction will compute  $R_s - R_t - 1$  instead of  $R_s - R_t$ .

B) The beq instruction will branch whenever  $R_s == R_t + 1$  instead of whenever  $R_s == R_t$ .

C) The slt instruction will set  $R_d$  to 1 whenever  $R_s < R_t + 1$  instead of whenever  $R_s < R_t$ .

### Problem 3

A modular 1-bit adder:

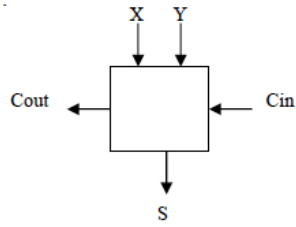

Truth table for the 1-bit adder:

X	Y	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Karnaugh map for S:



S		YCin			
		00	01	11	10
X	0	0	1	0	1
	1	1	0	1	0

$$S = \overline{X}Y\overline{Cin} + \overline{X}Y\overline{Cin} + X\overline{Y}\overline{Cin} + XY\overline{Cin}$$


Karnaugh map for Cout:

Cout		YCin			
		00	01	11	10
X	0	0	0	1	0
	1	0	1	1	1

$$Cout = YCin + XY + XCin$$

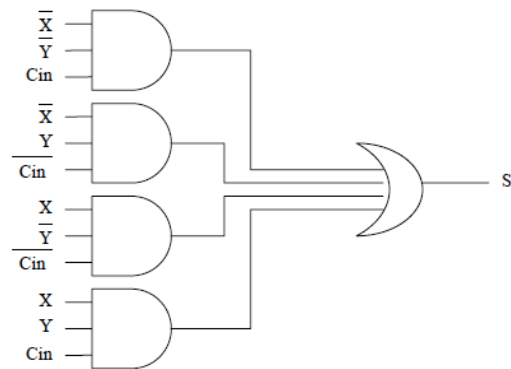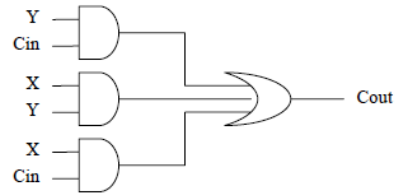

4-bit adder:

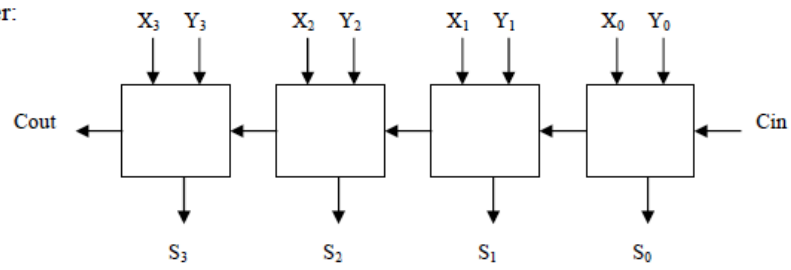

## problem 4

