

EE116C/CS151B



Fall 2017

Instructor: Professor Lei He
TA: Yuan Liang

Review

- **Arithmetic Logic Unit (ALU) Design**

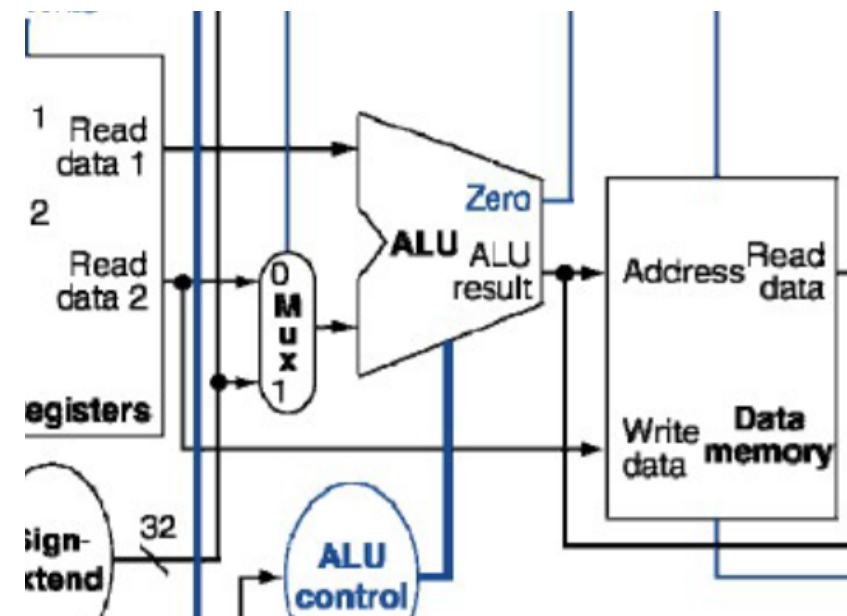 - Input: two operand (32-bits), ALU control signal
- Output: Zero, ALU results, overflow, carryout



Review

- **Arithmetic Logic Unit (ALU) Design**

- Function:


- Add
 - Subtract
 - Overflow dealing
 - And
 - Or
 - Branch
 - Set-On-Less-Than (SLT)

- **How?**

Review

- **1-bit ALU**

 - Input: two operand (1-bits), ALU control signal, **carryin**
- Output: Zero, ALU results, ~~**overflow**~~, carryout




Operation?
and,
or,
add with carryin,
etc.

Review

- **1-bit ALU**

 - Input: two operand (1-bits), ALU control signal, **carryin**
- Output: Zero, ALU results, ~~**overflow**~~, carryout




Composed of AND, OR, NOT gates.

$$\text{CarryOut} = (b \ \& \ \text{CarryIn}) \mid (a \ \& \ \text{CarryIn}) \mid (a \ \& \ b)$$

$$\begin{aligned} \text{Sum} = & (!a \ \& \ !b \ \& \ \text{CarryIn}) \mid (!a \ \& \ b \ \& \ !\text{CarryIn}) \\ & \mid (a \ \& \ !b \ \& \ !\text{CarryIn}) \mid (a \ \& \ b \ \& \ \text{CarryIn}) \end{aligned}$$

Review

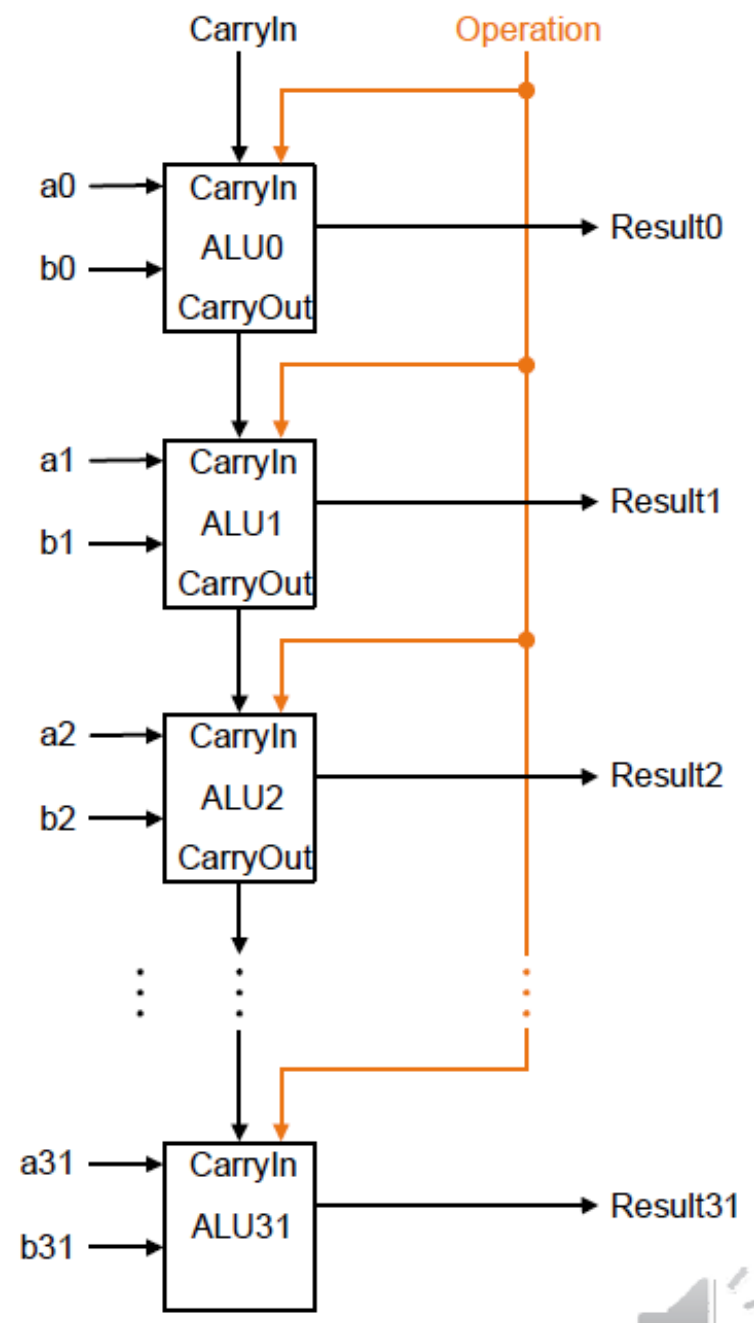- **Style 1: Ripple Carry Adder (1-bit ALU -> 32-bit ALU)**




- **Function:**

- **Add**
- Subtract
- Overflow dealing
- **And**
- **Or**
- Branch
- Set-On-Less-Than (SLT)

Review

- **Style 1: Ripple Carry Adder (1-bit ALU -> 32-bit ALU)**

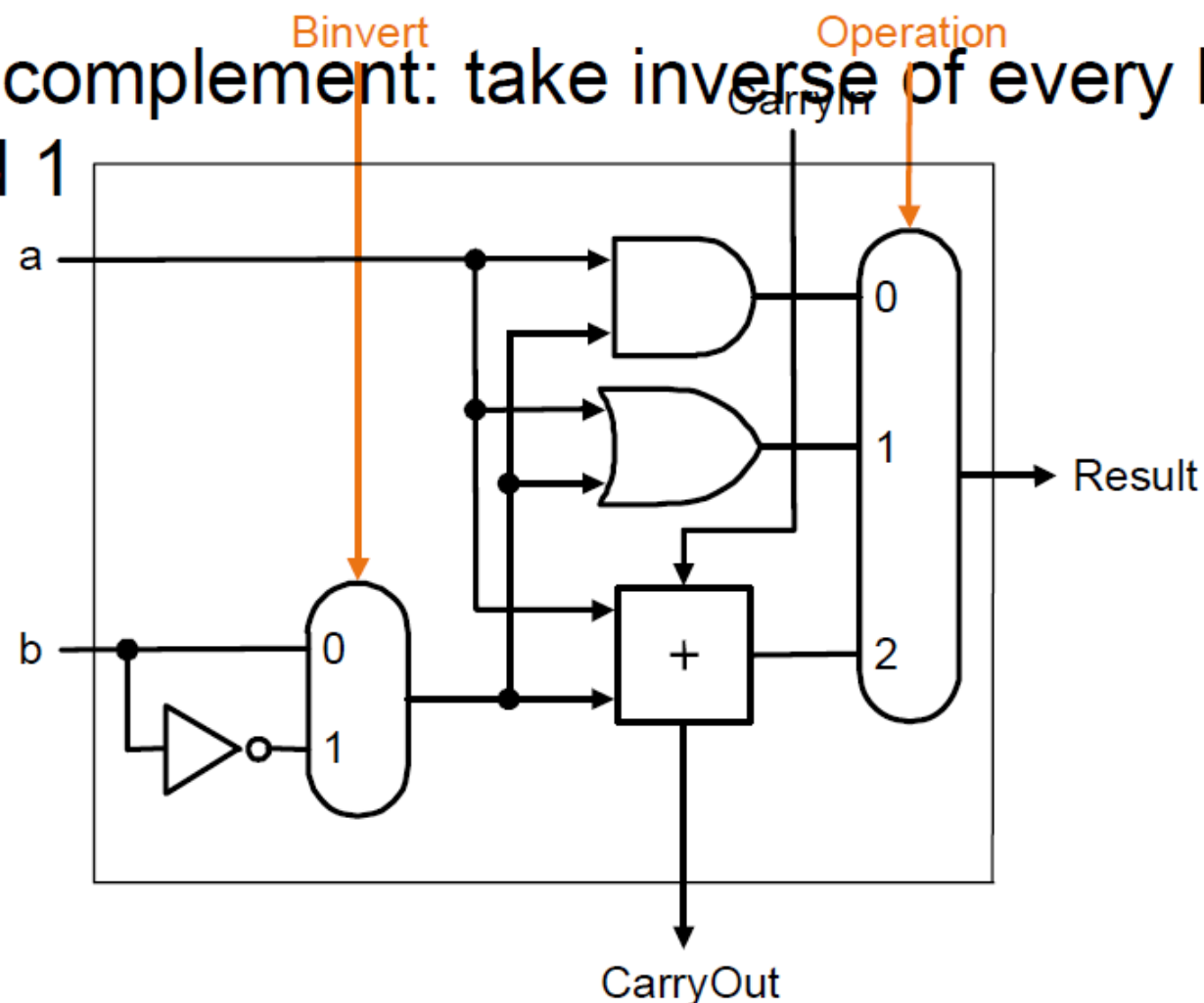2's complement: take inverse of every bit and add 1




- **Function:**

- **Add**
- **Subtract**
- Overflow dealing
- **And**
- **Or**
- Branch
- Set-On-Less-Than (SLT)

Review

- **Style 1: Ripple Carry Adder (1-bit ALU -> 32-bit ALU)**

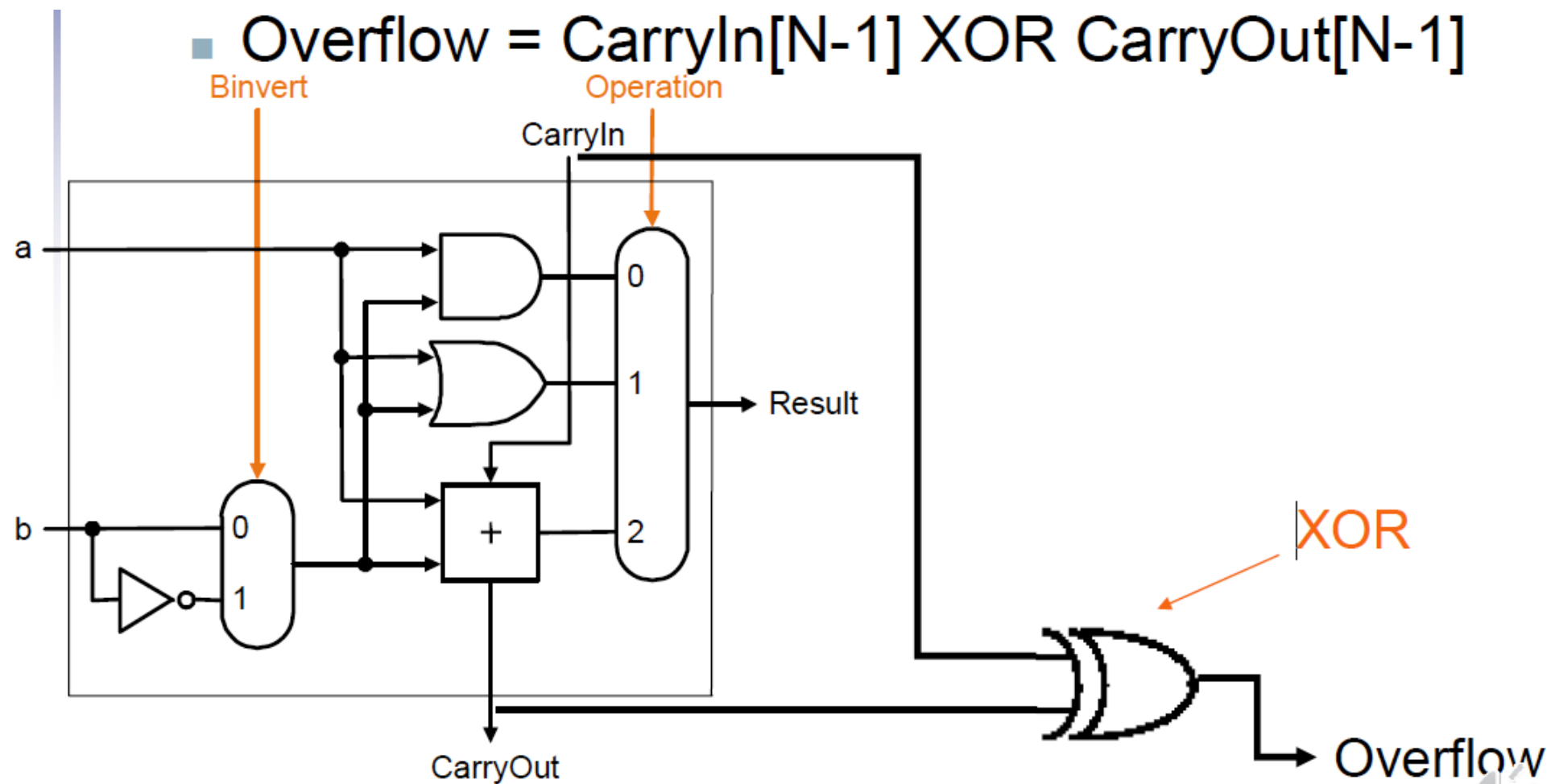- **Overflow = CarryIn[N-1] XOR CarryOut[N-1]**



- **Function:**

- **Add**
- **Subtract**
- **Overflow dealing**
- **And**
- **Or**
- Branch
- Set-On-Less-Than (SLT)

only for the most significant bit ALU

Review

- **Style 1: Ripple Carry Adder (1-bit ALU -> 32-bit ALU)**

- bneq r1, r2, L
- beq r1, r2, L
- if (a == b)
- if (a != b)
- -> a - b != 0

One big NOR gate including all N results.

if any result(i) == 1 -> return 0
if all result(i) == 0 -> return 1

- **Function:**

- **Add**
- **Subtract**
- **Overflow dealing**
- **And**
- **Or**
- **Branch**
- **Set-On-Less-Than (SLT)**

Review

- **Style 1: Ripple Carry Adder (1-bit ALU \rightarrow 32-bit ALU)**

- `slt rd, rs, rt`

- if ($rs < rt$) $rd = 1$

- else $rd = 0$

If $R[rs]$ is input A, and $R[rt]$ is input B, we can subtract, and then take the most significant bit of the result.

.If $MSB = 1$, then the difference is negative and thus $R[rs]$ is less than $R[rt]$

• Function:

- **Add**

- **Subtract**

- **Overflow dealing**

- **And**

- **Or**

- **Branch**

- **Set-On-Less-Than (SLT)**

Review

- **Style 1: Ripple Carry Adder (1-bit ALU -> 32-bit ALU)**

- **Function:**

- **Add**

- **Subtract**


- **Overflow dealing**

- **And**


- **Or**

- **Branch**

- **Set-On-Less-Than (SLT)**

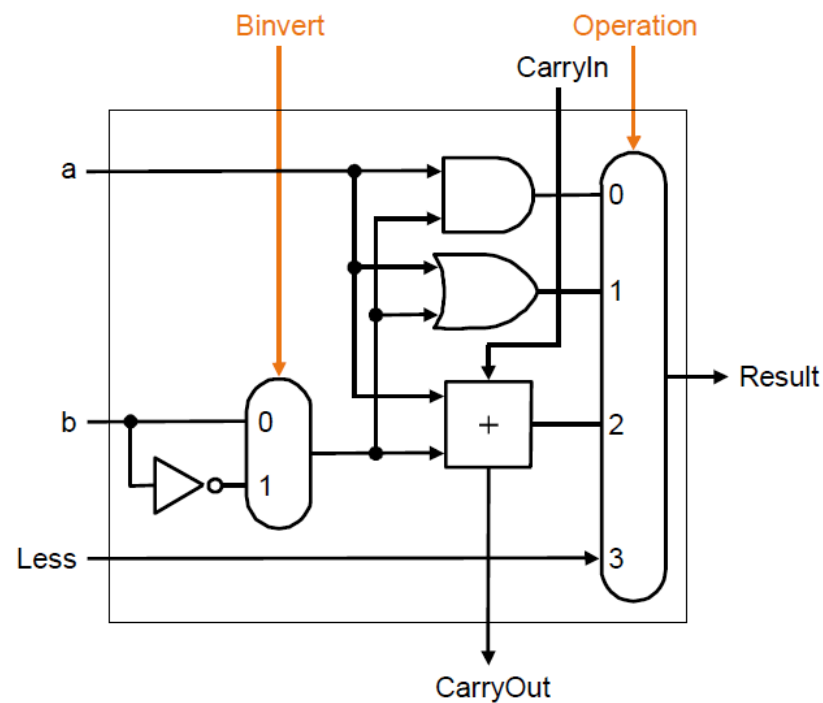


All but MSB

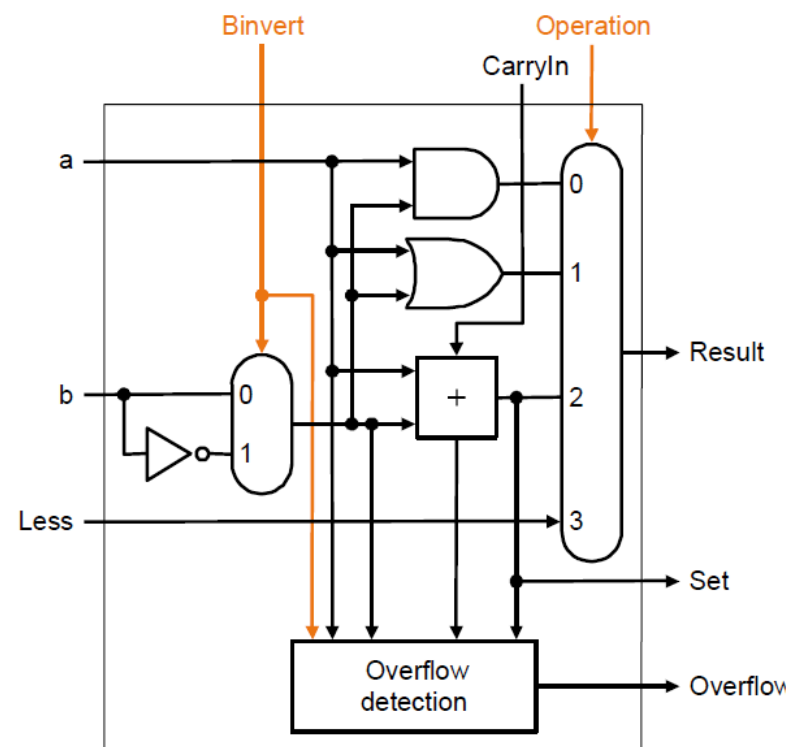

Most Significant Bit

Review

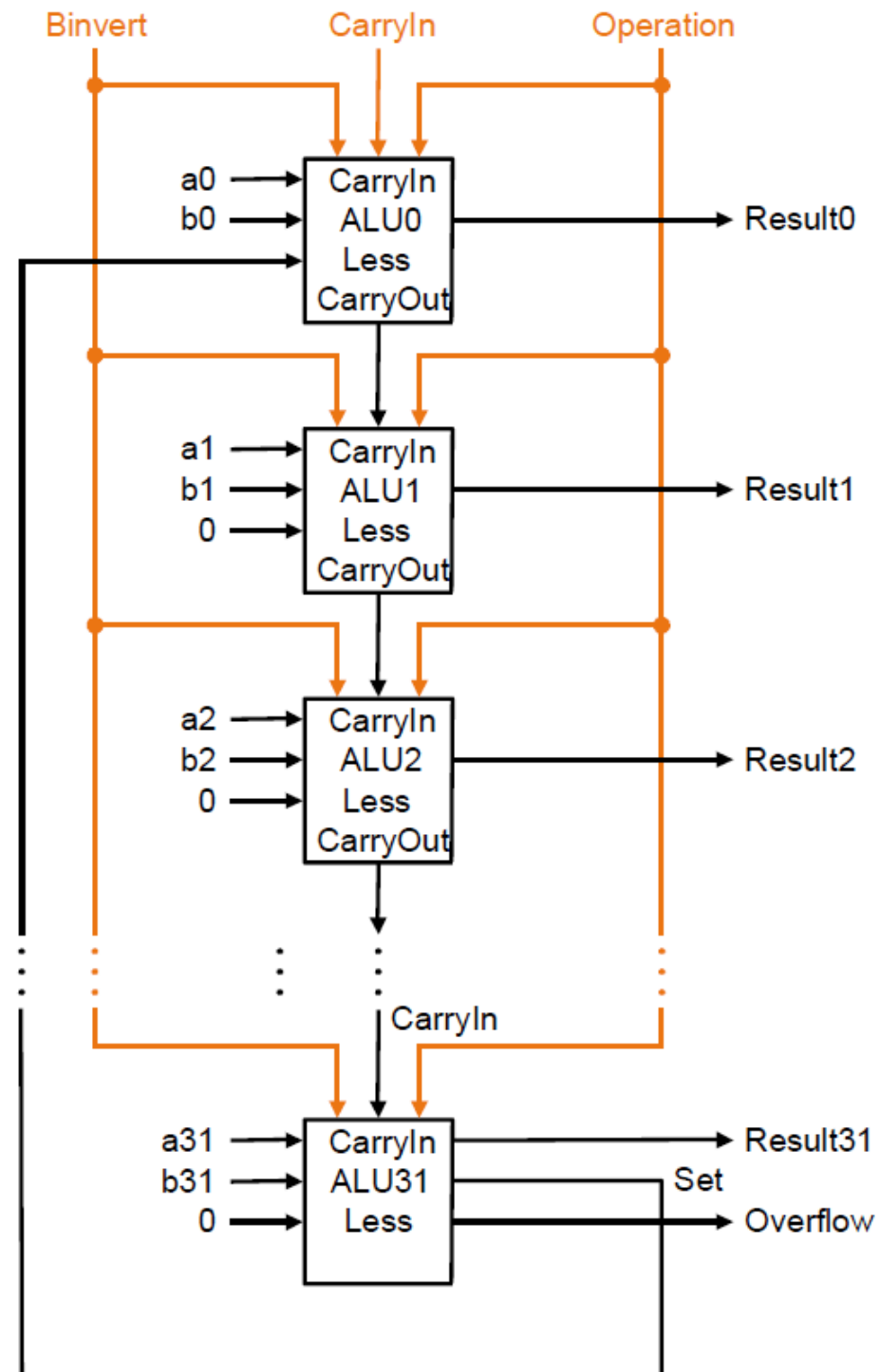- **Style 1: Ripple Carry Adder (1-bit ALU -> 32-bit ALU)**



- **Function:**

- **Add**

- **Subtract**

- **Overflow dealing**

- **And**

- **Or**


- **Branch**

- **Set-On-Less-Than (SLT)**

Review

- **Discussion: ripple style 32-bit adder**

 - Worst case delay for N-bit Ripple Carry Adder



$$\text{CarryOut} = (b \ \& \ \text{CarryIn}) \mid (a \ \& \ \text{CarryIn}) \mid (a \ \& \ b)$$

$$\text{Delay} = 2N$$

$$\begin{aligned} \text{Sum} = & (!a \ \& \ !b \ \& \ \text{CarryIn}) \mid (!a \ \& \ b \ \& \ !\text{CarryIn}) \\ & \mid (a \ \& \ !b \ \& \ !\text{CarryIn}) \mid (a \ \& \ b \ \& \ \text{CarryIn}) \end{aligned}$$

$$\text{Delay} = 2N$$

$$\text{Total delay} = 32 * 2N$$

Review

- **Style 2: Carry Lookahead Adder (1-bit ALU -> 32-bit ALU)**
 - The principle of the Carry Lookahead Adder is to sacrifice space and complexity in the interest of speed.
 - For calculating Cout, we will use two additional signals at 1-bit adder:
 - Generate (G_n) = $A_n * B_n$
 - Propagate (P_n) = $A_n \wedge B_n$

Review

- **Style 2: Carry Lookahead Adder (1-bit ALU -> 32-bit ALU)**

Ripple Carry Adder:

$$C1 = (A0 * B0) + (A0 * C0) + (B0 * C0)$$

$2T + 3T$


Carry Lookahead Adder:

$$G0 = A0 * B0$$

$$P0 = A0 \wedge B0$$


$$C1 = G0 + C0 * P0$$

$2T + 2T + 2T$

 

Review

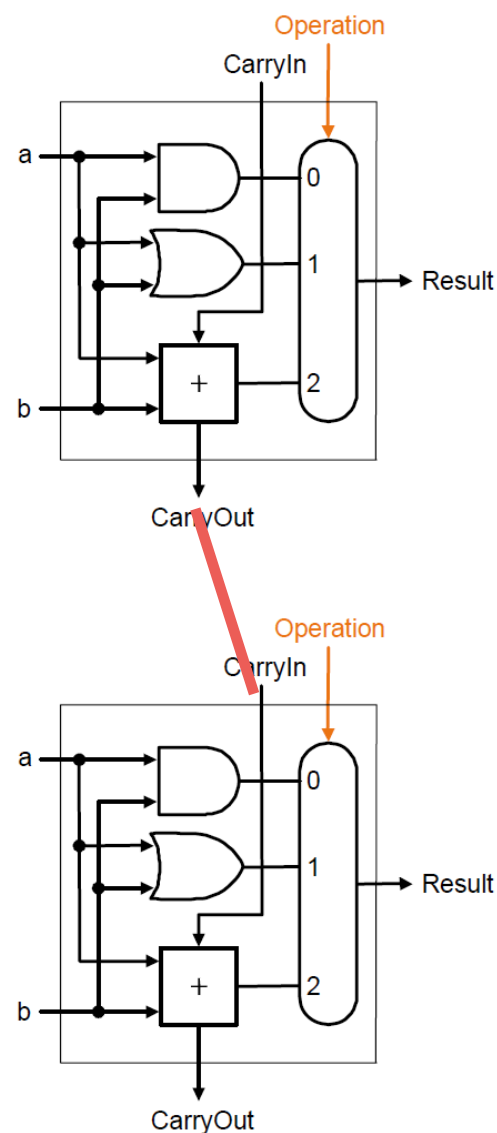- Style 2: Carry Lookahead Adder (1-bit ALU -> 32-bit ALU)**



Ripple Carry Adder:

$$C1 = (A0 * B0) + (A0 * C0) + (B0 * C0)$$

$$C2 = (A1 * B1) + (A1 * C1) + (B1 * C1)$$

$$2T + 3T + 2T + 3T$$

Carry Lookahead Adder:

$$G0 = A0 * B0$$

$$P0 = A0 \wedge B0$$

$$C1 = G0 + C0 * P0$$

$$G1 = A1 * B1$$

$$P1 = A1 \wedge B1$$


$$C1 = G1 + C1 * P1 = G1 + (G0 + C0 * P0) * P1$$

$$= G1 + G0 * P1 + C0 * P0 * P1$$

$$2T + 3T + 3T$$

Review

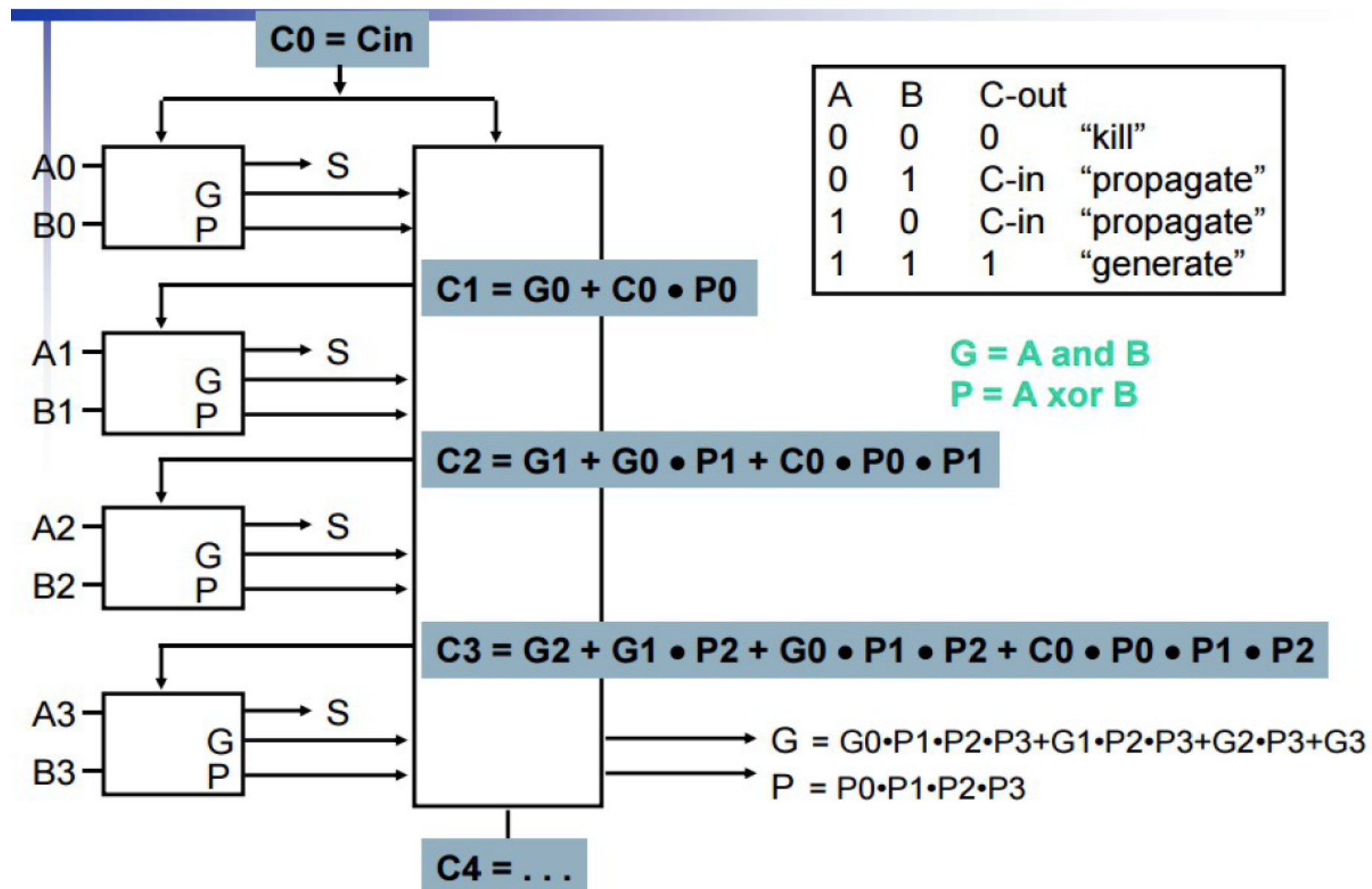
- **Style 2: Carry Lookahead Adder (1-bit ALU -> 32-bit ALU)**



Review

- **Style 2.1: [Partial] Carry Lookahead Adder**

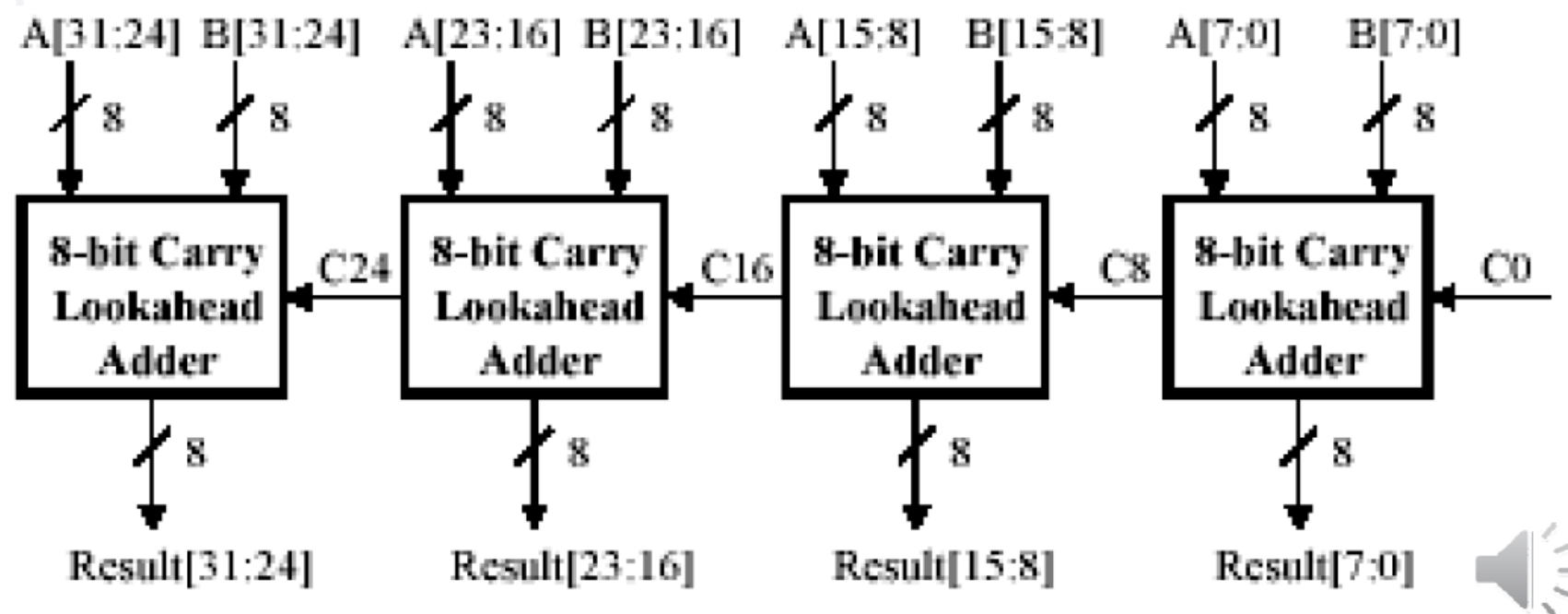- Connect several N-bit Lookahead Adders together
- Four 8-bit carry lookahead adders can form a 32-bit partial carry lookahead adder



Review

- **Style 2.2: [Hierarchical] Carry Lookahead Adder**

